

VDD VSS RX

BISHOP FOX


By Tastic

microSD Transflash1




LCD Screw Terminal

Arduino Nano 3.0

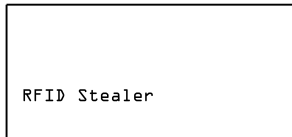

RFID Stealer

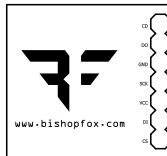

CD
D0
GND
SCK
VCC
D5
CS



300uF 50V



R2 - 2000Ω



R1 - 250Ω



LM317LZJ



3.6V Battery

+
-